

CSU22022 Computer Architecture I

Thirteenth Lecture - Micro-operations

Michael Manzke

2023-2024

Trinity College Dublin

Micro-ops	Description
$R0 \leftarrow \overline{R1}$	Logical bitwise NOT (1's compliment)
$R0 \leftarrow R1 \wedge R2$	Logical bitwise AND (clears bits)
$R0 \leftarrow R1 \vee R2$	Logical bitwise OR (sets bits)
$R0 \leftarrow R1 \oplus R2$	Logical bitwise XOR (complements bits)

Table 1: The aim here is to provide an effective set of bitwise functions. This is a typical basic set.

George Bode Prof. of mathematics in UCC introduced the notation ' \wedge ' and ' \vee ' in 1854, they are used in Register Transfer (RT) notation if it is necessary to distinguish addition from logical OR. For example:

 


Figure 1: The OR micro-ops will always use \vee .

Shift Micro-operations

These provide lateral bitwise shift which are essential for many basic arithmetic algorithms e.g., multiplication division , square root. . .

The minimal set is:

$$R \leftarrow srR \equiv R_i \leftarrow R_{i+1}, i = 0, n - 2, R_{n-1} \leftarrow 0 \quad (1)$$

$$R \leftarrow slR \equiv R_i \leftarrow R_{i-1}, i = 1, n - 1, R_0 \leftarrow 0 \quad (2)$$

These are logical shifts and from them you can develop variants which handle the end bits differently, e.g., arithmetic shift, rotates. . .

- Provide choice of path
- Two approaches are used:
 - Multiplexer-based transfer for speed
 - Bus-based transfers for flexibility and economy
 - We do not use Bus-based transfers in our processor design

Transfer with Multiplexer


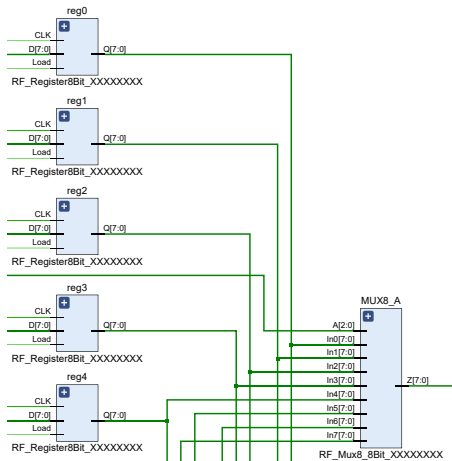


Figure 2: The address $A[2:0]$ allows us to select the source register for a transfer to the destination register.

- The arithmetic circuit may be implemented with the following components:
 - Ripple Carry Adder
 - from a cascade of full-adder circuits
 - The data input to the parallel adder is manipulated in order to achieve several arithmetic operations

n-bit Arithmetic Logic Unit(ALU)

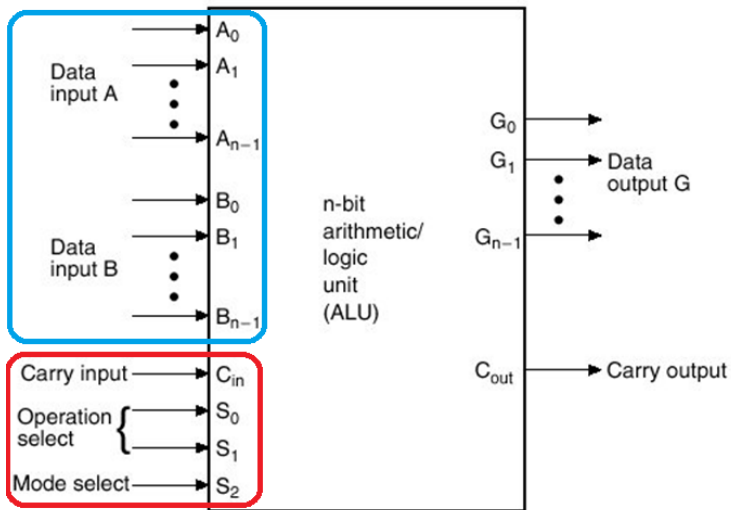

32-bit Arithmetic Logic Unit(ALU)

 


Figure 3: The ALU has four input signals C_{in} , S_0 , S_1 and S_2 that determine the operation of the unit. C_{in} , S_0 , S_1 is used for the BLogic and the Adder. Also, S_0 , S_1 determines the operation of the LogicCircuit. Both the adder and the LogicCircuit compute an output, but S_2 selects one output.

Signals S_1, S_0 select the Blogic Operation

 


Figure 4: Table?? depicts the Blogic Operation

Signals S_1, S_0 select the Logic Circuit Operation

 


Figure 5: The signals S_1, S_0 at the same time select the Logic Circuit Operation

The S_2 selects Adder or Logic Circuit

 


Figure 6: The signals S_2 selects the desired output, arithmetic or logic.