

CSU22022 Computer Architecture I

Tenth Lecture - Register Transfer

Michael Manzke

2023-2024

Trinity College Dublin

Register Transfer

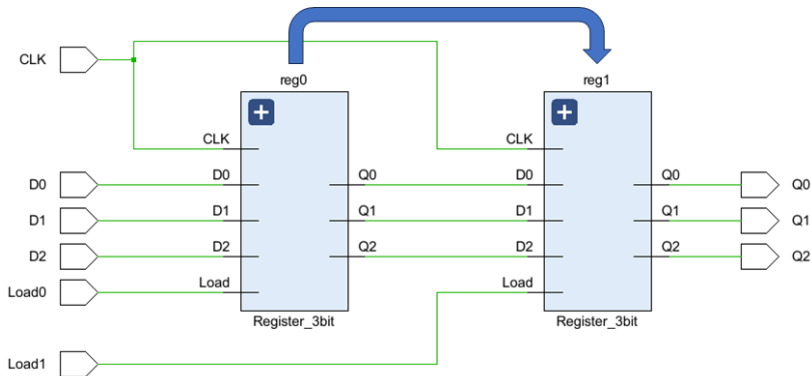


Figure 1: The schematic depicts a register transfer from reg0 to reg1

Two Register Transfer - One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Two_Register_3bit is
5     Port ( D0, D1, D2 : in STD_LOGIC;
6           Load0, Load1, CLK : in STD_LOGIC;
7           Q0, Q1, Q2 : out STD_LOGIC);
8 end Two_Register_3bit;
9
10 architecture Behavioral of Two_Register_3bit is
11
12     COMPONENT Register_3bit
13     Port ( D0, D1, D2 : in STD_LOGIC;
14           CLK, Load : in STD_LOGIC;
15           Q0, Q1, Q2 : out STD_LOGIC);
16     END COMPONENT;
```

Listing 1: The Two_Register_3bit entity

Two Register Transfer - Two

```
1  signal reg0toreg1_bit0, reg0toreg1_bit1, reg0toreg1_bit2
   : std_logic;
2  -- Propagation Delay according to StdentID e.g. 26 33
   57 25(DEC)
3  constant AND_gate_delay : Time := 6ns; -- 6=5+1
4  constant NAND_gate_delay : Time := 3ns;-- 3=2+1
5  constant OR_gate_delay : Time := 8ns; -- 8=7+1
6  constant NOR_gate_delay : Time := 6ns; -- 6=5+1
7  constant XOR_gate_delay : Time := 4ns; -- 4=3+1
8  constant XNOR_gate_delay : Time := 4ns;-- 4=3+1
9  constant NOT_gate_delay : Time := 7ns; -- 7=6+1
```

Listing 2: The signals reg0toreg1_bit0 reg0toreg1_bit1 and reg0toreg1_bit2 connect reg0 with reg1

Two Register Transfer - Three

```
1 begin
2
3     reg0: Register_3bit PORT MAP (
4         D0 => D0, D1 => D1, D2 => D2,
5         CLK => CLK,
6         Load => Load0,
7         Q0 => reg0toreg1_bit0, Q1 => reg0toreg1_bit1,
8         Q2 => reg0toreg1_bit2);
9
10    reg1: Register_3bit PORT MAP (
11        D0 => reg0toreg1_bit0, D1 => reg0toreg1_bit1,
12        D2 => reg0toreg1_bit2,
13        CLK => CLK,
14        Load => Load1,
15        Q0 => Q0, Q1 => Q1, Q2 => Q2);
16
17 end Behavioral;
```

Listing 3: The Register_3bit entity is instantiated twice (reg0 and reg1)

Register with three D Flip Flops

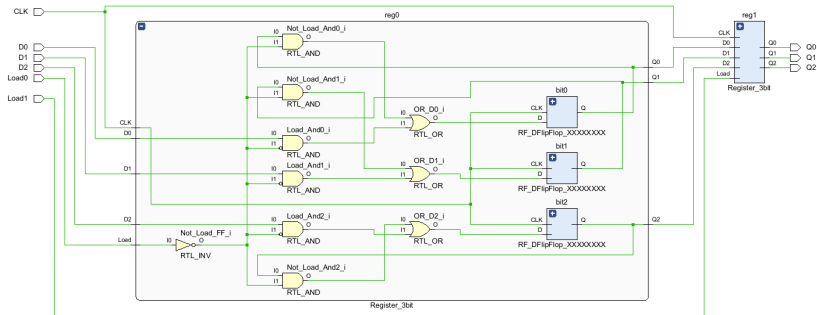


Figure 2: The schematic depicts registers reg0 and reg1. The register instantiates three D Flip Flops including **Load logic**

Register Implementation - One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Register_3bit is
5     Port ( D0, D1, D2 : in STD_LOGIC;
6           CLK, Load : in STD_LOGIC;
7           Q0, Q1, Q2 : out STD_LOGIC);
8 end Register_3bit;
9
10 architecture Behavioral of Register_3bit is
11
12     COMPONENT RF_DFlipFlop_XXXXXXX
13     Port ( CLK, D, Load : in STD_LOGIC;
14           Q : out STD_LOGIC);
15     END COMPONENT;
```

Listing 4: Register_3bit entity

Register Implementation - Two

```
1  signal Q_bit0, Q_bit1, Q_bit2 : std_logic;
2  signal OR_D0, OR_D1, OR_D2 : std_logic;
3  signal Not_Load_FF, Load_FF : std_logic;
4  signal Not_Load_And0, Not_Load_And1, Not_Load_And2:
   std_logic;
5  signal Load_And0, Load_And1, Load_And2: std_logic;
6
7  -- Propagation Delay according to StdentID e.g. 26 33
   57 25(DEC)
8  constant AND_gate_delay : Time := 6ns; -- 6 =5+1
9  constant NAND_gate_delay : Time := 3ns;-- 3=2+1
10 constant OR_gate_delay : Time := 8ns;  -- 8=7+1
11 constant NOR_gate_delay : Time := 6ns; -- 6=5+1
12 constant XOR_gate_delay : Time := 4ns; -- 4=3+1
13 constant XNOR_gate_delay : Time := 4ns;-- 4=3+1
14 constant NOT_gate_delay : Time := 7ns; -- 7=6+1
```

Listing 5: signals and constants

Register Implementation - Three

```
1 begin
2
3     Not_Load_FF <= not Load after NOT_gate_delay;
4     Load_FF <= not Not_Load_FF after NOT_gate_delay;
5
6     -- Instantiate the least significant bit
7     bit0: RF_DFlipFlop_XXXXXXX PORT MAP (
8         CLK => CLK, D => OR_D0, Q => Q_bit0 );
9
10    Not_Load_And0 <= Q_bit0 and Not_Load_FF after
11        AND_gate_delay;
12    OR_D0 <= Not_Load_And0 or Load_And0 after OR_gate_delay;
13    Load_And0 <= D0 and Load_FF after AND_gate_delay;
14    Q0 <= Q_bit0;
15
16    bit1: RF_DFlipFlop_XXXXXXX PORT MAP (
17        CLK => CLK, D => OR_D1, Q => Q_bit1 );
```

Listing 6: The Register_3bit entity instantiates three D Flip Flops

Register Implementation - Four

```
1    Not_Load_And1 <= Q_bit1 and Not_Load_FF after
    AND_gate_delay;
2    OR_D1 <= Not_Load_And1 or Load_And1 after OR_gate_delay;
3    Load_And1 <= D1 and Load_FF after AND_gate_delay;
4    Q1 <= Q_bit1;
5
6    -- Instantiate the most significant bit
7    bit2: RF_DFlipFlop_XXXXXXX PORT MAP (
8        CLK => CLK, D => OR_D2, Q => Q_bit2);
9
10   Not_Load_And2 <= Q_bit2 and Not_Load_FF after
    AND_gate_delay;
11   OR_D2 <= Not_Load_And2 or Load_And2 after OR_gate_delay;
12   Load_And2 <= D2 and Load_FF after AND_gate_delay;
13   Q2 <= Q_bit2;
14
15 end Behavioral;
```

Listing 7: The Register_3bit entity instantiates three D Flip Flops

Register with three D Flip Flops and Load signal

 


Figure 3: The schematic depicts the gate logic of one D Flip Flops

New D Flip Flop Version

 


Figure 4: This D Flip Flops has no Q_not port

D Flip Flop Implementation - One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity RF_DFlopFlop_XXXXXXX is
5     Port ( CLK, D : in STD_LOGIC;
6           Q : out STD_LOGIC);
7 end RF_DFlopFlop_XXXXXXX;
```

Listing 8: RF_DFlopFlop_XXXXXXX entity

D Flip Flop Implementation - Two

```
1 architecture Behavioral of RF_DFlipFlop_XXXXXXX is
2
3     signal Q_t, Q_not_t, X, S, R, Y, Z : std_logic;
4
5     -- Propagation Delay according to StdentID e.g. 26 33 57
6     25(DEC)
7
8     constant AND_gate_delay : Time := 6ns;      -- 6 = 5 + 1
9     constant NAND_gate_delay : Time := 3ns;     -- 3 = 2 + 1
10    constant OR_gate_delay : Time := 8ns;       -- 8 = 7 + 1
11    constant NOR_gate_delay : Time := 6ns;      -- 6 = 5 + 1
12    constant XOR_gate_delay : Time := 4ns;      -- 4 = 3 + 1
13    constant XNOR_gate_delay : Time := 4ns;     -- 4 = 3 + 1
14    constant NOT_gate_delay : Time := 7ns;      -- 7 = 6 + 1
```

Listing 9: signals and constants

D Flip Flop Implementation - Three

```
1 begin
2
3     X <= Y nand S after NAND_gate_delay;
4     S <= X nand CLK after NAND_gate_delay;
5     Z <= S and CLK after AND_gate_delay;
6     R <= Z nand Y after NAND_gate_delay;
7     Y <= R nand D after NAND_gate_delay;
8     Q_t <= S nand Q_not_t after NAND_gate_delay;
9     Q_not_t <= R nand Q_t after NAND_gate_delay;
10    Q <= Q_t;
11
12 end Behavioral;
```

Listing 10: The **architecture** with Load port and Q_not port removed

Register Load Logic

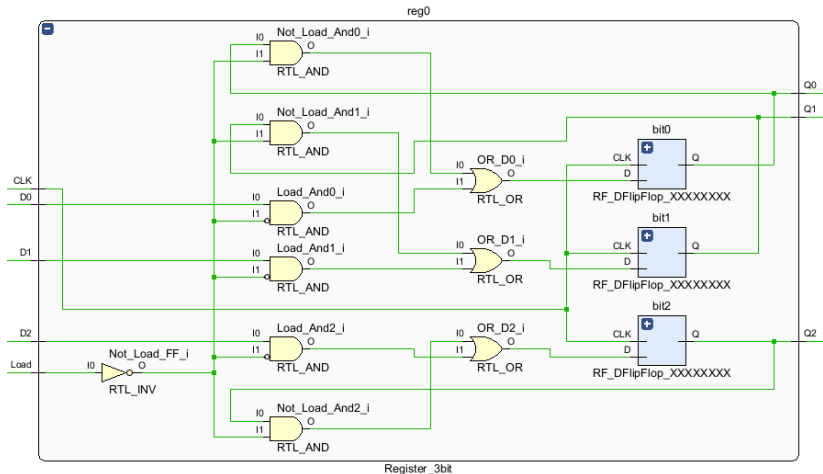


Figure 5: The logic puts the flip flop output Q back to its input D if the load signal is not set. 16/18

Two Register Transfer Timing Diagram - One

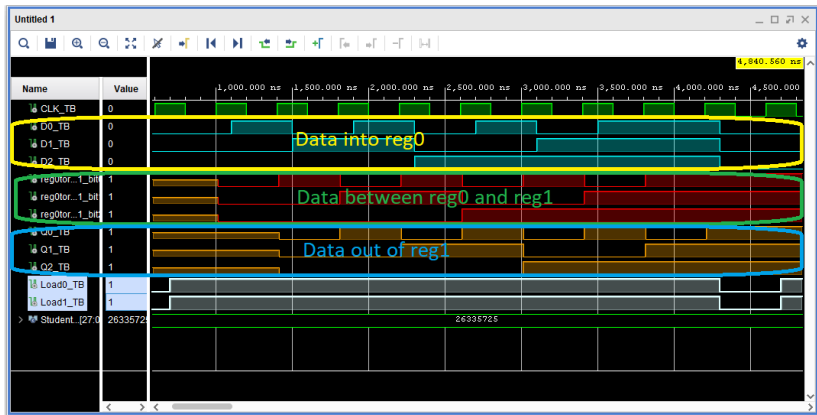


Figure 6: This timing diagram depicts 3-bit values going into reg0, 3-bit values between reg0 and reg1, and 3-bit values at the output of reg1.

Two Register Transfer Timing Diagram - Two

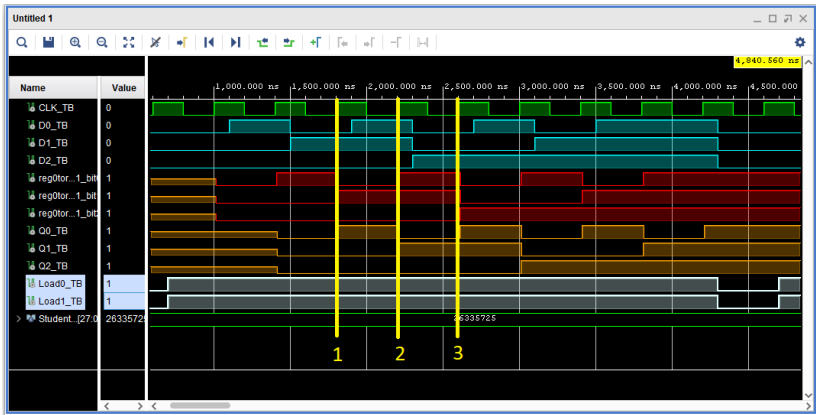


Figure 7: At every rising edge of the clock, we can observe how 3-bit values move from the input of reg0 to its output and at the same time the 3-bit values between the registers move to the output of reg1.