

CSU22022 Computer Architecture I

Eleventh Lecture - RTL

Michael Manzke

2023-2024

Trinity College Dublin

Register Transfer


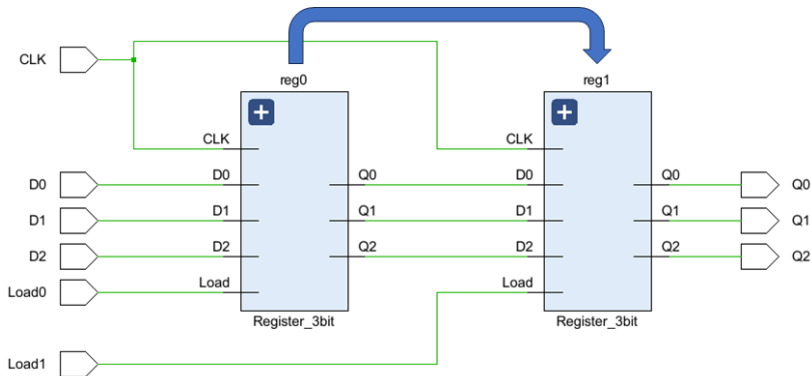


Figure 1: The schematic depicts a register transfer from reg0 to reg1

- Describing large-scale processor activity
- To discuss digital systems of this scale and level of complexity:
 - We need a number of descriptive tools
- For example:
 - Circuit schematics highlight the circuit components and their connectivity

Register Transfer Specification

 - Source Register
- Destination Register
- Operation to be applied
- Condition or control function under which the transfer will occur
 - We assume synchronous operation and omit the clock



Building Register-Transfer Statements

Symbol(s)	Description	Examples
Letters and Numerals	Denote Registers	AR, DR, R2, IR
Parentheses	Denote sections of Registers	R2(9), AR(2), R1(7:0)
Arrow	Denotes data transfer	R1<-R2 IR<-DR
Comma	Separates simultaneous transfers	R1<-R2, R3<-AR
Square bracket	Denote memory addressing	DR<-M[AR] (a read) M[AR]<-DR (a write)

Operation	RTL	VHDL	CSU22022
Combinational Assignment	=	<= (CSA)	
Register Transfer	←	<= (CSA)	
Addition	+	+	we don't use it!
Subtraction	-	-	we don't use it!
Bitwise AND	∧	and	
Bitwise OR	∨	or	
Bitwise XOR	⊕	xor	
Bitwise NOT	-	not	

Table 1: Logical operations

Operation	RTL	VHDL	CSU22022
Shift left (logical)	sl	sll	we don't use it!
Shift right (logical)	sr	srl	we don't use it!
Vector/Register	A(3:0)	A(3 downto 0)	
Concatenation		&	

Table 2: Logical operations

- A micro-operation is an operation which can be accomplished:
 - Within a small number of gate propagation delays
 - Upon data stored in adjacent registers and memory
- Those commonly encountered in digital systems divide naturally into four groups:
 - Transfer or identity micro-ops copy data
 - e.g., $R1 \leftarrow R2$, $DR \leftarrow M[AR]$
 - Arithmetic micro-ops provide the elements of arithmetic
 - e.g. $R0 \leftarrow R1 + R2$
 - Logic micro-ops provide per bit operations
 - e.g. $R1 \leftarrow R2 \text{ or } R2$
 - Shift micro-ops provide bit rotations
 - e.g. $R1 \leftarrow sr R2$, $R0 \leftarrow rol R1$

Arithmetic Micro-ops - Adder

Let R0, R1, and R3 be n -bit Register and consider what can be done with an n -bit Adder:

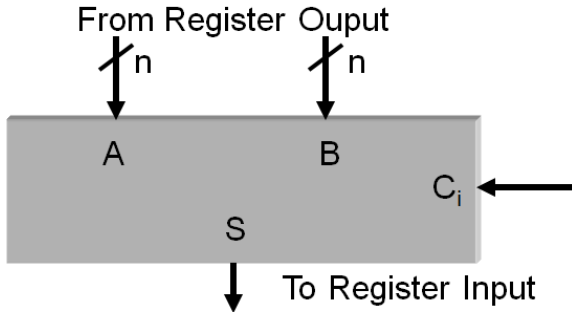


Figure 2: n -bit Adder

Full Adder - See Seventh lecture

 


Figure 3: Implementation of a Full Adder with Two Half Adders and an OR Gate

Full Adder VHDL Code - One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Full_Adder is
5     Port ( x : in STD_LOGIC;
6           y : in STD_LOGIC;
7           c_in : in STD_LOGIC;
8           s : out STD_LOGIC;
9           C_out : out STD_LOGIC);
10 end Full_Adder;
```

Listing 1: entity Full_Adder

Full Adder VHDL Code - Two

```
1 architecture Behavioral of Full_Adder is
2     signal s0, s1, s2 : std_logic;
3     -- Propagation Delay according to StdentID e.g. 26 33
4     -- 57 25(DEC)
5     constant AND_gate_delay : Time := 6ns; -- least
6     -- significant digit 6=5+1
7     constant NAND_gate_delay : Time := 3ns; -- next more
8     -- significant digit 3=2+1
9     constant OR_gate_delay : Time := 8ns; -- next more
10    -- significant digit 8=7+1
11    constant NOR_gate_delay : Time := 6ns; -- next more
12    -- significant digit 6=5+1
13    constant XOR_gate_delay : Time := 4ns; -- next more
14    -- significant digit 4=3+1
15    constant XNOR_gate_delay : Time := 4ns; -- next more
16    -- significant digit 4=3+1
17    constant NOT_gate_delay : Time := 7ns; -- next more
18    -- significant digit 7=6+1
```

Listing 2: signals and constants

Full Adder VHDL Code - Three

```
1 begin
2
3     s0 <= x XOR y after XOR_gate_delay;
4     s1 <= x And Y after AND_gate_delay;
5     s2 <= s0 AND c_in after AND_gate_delay;
6     s <= s0 XOR c_in after XOR_gate_delay;
7     c_out <= s2 OR s1;
8
9 end Behavioral;
```

Listing 3: Concurrent signal assignment statements

8-bit Ripple Adder

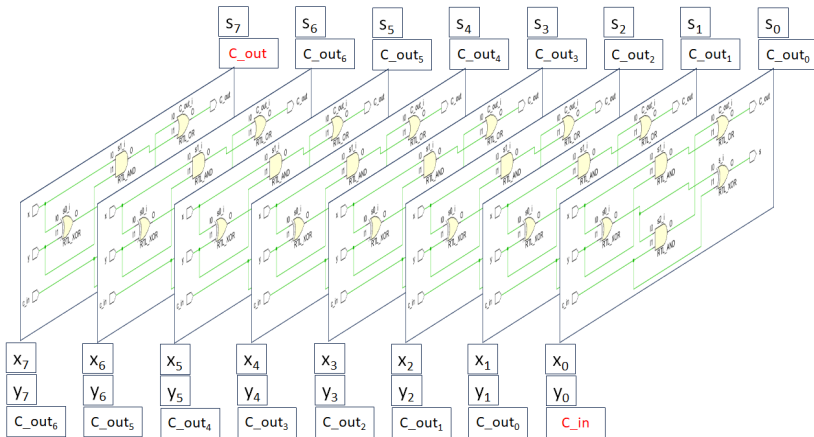


Figure 4: c_out from the less significant bit becomes the c_in for the next more significant bit.

Full 8-bit Ripple Adder VHDL Code - One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity RippleCarryAdder8_bit is
5     Port ( x, y : in STD_LOGIC_VECTOR (7 downto 0);
6           c_rca_in : in STD_LOGIC;
7           s : out STD_LOGIC_VECTOR (7 downto 0);
8           c_rca_out : out STD_LOGIC);
9 end RippleCarryAdder8_bit;
```

Listing 4: entity Full_Addder

Full 8-bit Ripple Adder VHDL Code - Two

```
1 architecture Behavioral of RippleCarryAdder8_bit is
2
3     COMPONENT Full_Adder
4     Port ( x : in STD_LOGIC;
5           y : in STD_LOGIC;
6           c_in : in STD_LOGIC;
7           s : out STD_LOGIC;
8           c_out : out STD_LOGIC);
9     END COMPONENT;
```

Listing 5: COMPONENT declaration

Full 8-bit Ripple Adder VHDL Code - Three

```
1  signal c_out0, c_out1, c_out2, c_out3 : std_logic;
2  signal c_out4, c_out5, c_out6 : std_logic;
3
4  -- Propagation Delay according to StdentID e.g. 26 33
   57 25(DEC)
5  constant AND_gate_delay : Time := 6ns; -- least
   significant digit 6 =5+1
6  constant NAND_gate_delay : Time := 3ns;-- next more
   significant digit 3=2+1
7  constant OR_gate_delay : Time := 8ns;  -- next more
   significant digit 8=7+1
8  constant NOR_gate_delay : Time := 6ns; -- next more
   significant digit 6=5+1
9  constant XOR_gate_delay : Time := 4ns; -- next more
   significant digit 4=3+1
10 constant XNOR_gate_delay : Time := 4ns;-- next more
   significant digit 4=3+1
11 constant NOT_gate_delay : Time := 7ns; -- next more
   significant digit 7=6+1
```

Listing 6: signals and constants

Full 8-bit Ripple Adder VHDL Code - Four

```
1  -- Instantiate the least significant bit
2  bit0: Full_Adder PORT MAP (
3      x => x(0),
4      y => y(0),
5      c_in => c_rca_in,
6      s => s(0),
7      c_out => c_out0
8  );
9
10 bit1: Full_Adder PORT MAP (
11     x => x(1),
12     y => y(1),
13     c_in => c_out0,
14     s => s(1),
15     c_out => c_out1
16 );
```

Listing 7: Instantiate Full_Adders for bit0 and bit1

Full 8-bit Ripple Adder VHDL Code - Five

```
1  -- Instantiate the least significant bit
2  bit2: Full_Adder PORT MAP (
3      x => x(2),
4      y => y(2),
5      c_in => c_out1,
6      s => s(2),
7      c_out => c_out2
8  );
9
10 bit3: Full_Adder PORT MAP (
11     x => x(3),
12     y => y(3),
13     c_in => c_out2,
14     s => s(3),
15     c_out => c_out3
16 );
```

Listing 8: Instantiate Full_Adders for bit2 and bit3

Full 8-bit Ripple Adder VHDL Code - Six

```
1      -- Instantiate the least significant bit
2      bit4: Full_Adder PORT MAP (
3          x => x(4),
4          y => y(4),
5          c_in => c_out3,
6          s => s(4),
7          c_out => c_out4
8      );
9
10     bit5: Full_Adder PORT MAP (
11         x => x(5),
12         y => y(5),
13         c_in => c_out4,
14         s => s(5),
15         c_out => c_out5
16     );
```

Listing 9: Instantiate Full_Adders for bit4 and bit5

Full 8-bit Ripple Adder VHDL Code - Seven

```
1  -- Instantiate the least significant bit
2  bit5: Full_Adder PORT MAP (
3      x => x(5),
4      y => y(5),
5      c_in => c_out4,
6      s => s(5),
7      c_out => c_out5
8  );
9
10 bit6: Full_Adder PORT MAP (
11     x => x(6),
12     y => y(6),
13     c_in => c_out5,
14     s => s(5),
15     c_out => c_out6
16 );
```

Listing 10: Instantiate Full_Adders for bit6 and bit7

8-bit Ripple Adder Schematic

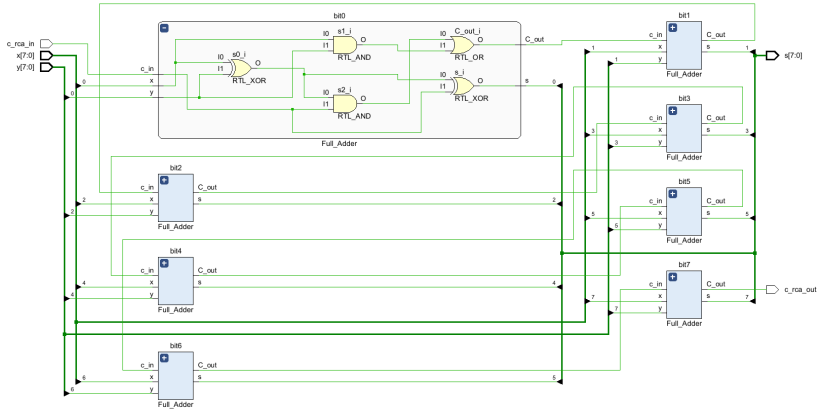


Figure 5: Schematic with detail for the least significant bit.

Conditioned use of an Adder

Operation	A	B	C	Function
$R0 \leftarrow R1 + R2$	R1	R2	0	Addition
$R0 \leftarrow R1 - R2$	R1	$\overline{R2}$	1	Subtraction
$R0 \leftarrow R1 + 1$	R1	0...0	1	Increment
$R0 \leftarrow R1 - 1$	R1	1...1	0	Decrement
$R0 \leftarrow \overline{R2}$	0...0	$\overline{R2}$	0	1's Complement
$R0 \leftarrow \overline{R2} + 1$	0...0	$\overline{R2}$	1	2's Complement

Table 3: By conditioning what arrives at A,B, and C we can achieve the above