

CSU22022 Computer Architecture I

Sixteenth Lecture - Binary Multiplier

Michael Manzke

2023-2024

Trinity College Dublin

Shift-and-Add Multiply

We will consider a shift-and-add multiply circuit as an example datapath.

$$P = A \times B$$

Product = Multiplier \times Multiplicand

Figure 1: A, B and P are n-bit unsigned integers.

Bit Products

$$P_i \quad i=0, n-1$$

$$P_i = a_i \times B = \begin{cases} 0 & \text{if } a_i=0 \\ B & \text{if } a_i=1 \end{cases} = a_i \wedge B$$

$$PP_j = \sum_{i=0}^j P_i \times 2^i = P_j \times 2^j + PP_{j-1}$$

$$P = PP_{n-1}$$

Figure 2: We can generate the bit products.

Multiplication Example

23 10111 Multiplicand

19 10011 Multiplier

10111

$\leftarrow P_0$

10111

$\leftarrow P_1 \times 2^1$

00000

$\leftarrow P_2 \times 2^2$

00000

$\leftarrow P_3 \times 2^3$

10111

$\leftarrow P_4 \times 2^4$

437

110110101

Product

Shift-and-Add Multiply Example

| Mutiplicand | | | | | | | | | | Multiplier | | | | | | | | | | | | | | |
|-------------------|----|----|----|----|----|----|----|----|----|----------------|--|--|--|--|------------------------------------|--|--|--|--|--|--|--|--|--|
| B4 B3 B2 B1 B0 | | | | | | | | | | Q4 Q3 Q2 Q1 Q0 | | | | | | | | | | | | | | |
| 1 0 1 1 1 (23) | | | | | | | | | | 1 0 0 1 1 (19) | | | | | | | | | | | | | | |
| 1 0 1 1 1 | | | | | | | | | | 1 0 0 1 1 | | | | | P0 | | | | | | | | | |
| 1 0 1 1 1 | | | | | | | | | | 1 0 0 1 1 | | | | | P1 x2^1 | | | | | | | | | |
| 0 0 0 0 0 | | | | | | | | | | 1 0 0 1 1 | | | | | P2 x2^2 | | | | | | | | | |
| 0 0 0 0 0 | | | | | | | | | | 1 0 0 1 1 | | | | | P3 x2^3 | | | | | | | | | |
| 1 0 1 1 1 | | | | | | | | | | 1 0 0 1 1 | | | | | P4 x2^4 | | | | | | | | | |
| 1 1 0 1 1 0 1 0 1 | | | | | | | | | | | | | | | P0+P1 x2^1+P2 x2^2+P3 x2^3+P1 x2^4 | | | | | | | | | |
| A9 | A8 | A7 | A6 | A5 | A4 | A3 | A2 | A1 | A0 | | | | | | | | | | | | | | | |
| Product | | | | | | | | | | | | | | | | | | | | | | | | |

Shift-and-Add Multiply Example

| Multiplicand | | | | | | | | | | Multiplier | | | | | | | | | | | | | | |
|-------------------|--|--|--|--|--|--|--|--|--|----------------|--|--|--|--|------------------------------------|--|--|--|--|--|--|--|--|--|
| B4 B3 B2 B1 B0 | | | | | | | | | | Q4 Q3 Q2 Q1 Q0 | | | | | | | | | | | | | | |
| 1 0 1 1 1 (23) | | | | | | | | | | 1 0 0 1 1 (19) | | | | | | | | | | | | | | |
| 0 0 0 0 0 | | | | | | | | | | | | | | | Initial partial product | | | | | | | | | |
| 1 0 1 1 1 | | | | | | | | | | 1 0 0 1 1 | | | | | P0 | | | | | | | | | |
| 1 0 1 1 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Q0 = 1 -> Add | | | | | | | | | |
| 1 0 0 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Shift | | | | | | | | | |
| 0 0 0 0 0 | | | | | | | | | | 1 0 0 1 1 | | | | | P0+P1 x2^1 | | | | | | | | | |
| 1 0 0 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Shift | | | | | | | | | |
| 0 0 0 0 0 | | | | | | | | | | 1 0 0 1 1 | | | | | P0+P1 x2^1+P2 x2^2 | | | | | | | | | |
| 1 0 0 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Q2 = 0 -> Shift | | | | | | | | | |
| 0 0 0 0 0 | | | | | | | | | | 1 0 0 1 1 | | | | | Shift | | | | | | | | | |
| 1 0 0 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | P0+P1 x2^1+P2 x2^2+P3 x2^3 | | | | | | | | | |
| 1 0 1 1 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Q3 = 0 -> Shift | | | | | | | | | |
| 1 1 0 1 1 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Shift | | | | | | | | | |
| 1 1 0 1 1 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | P0+P1 x2^1+P2 x2^2+P3 x2^3+P1 x2^4 | | | | | | | | | |
| 1 1 0 1 1 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | Q1 = 1 -> Add | | | | | | | | | |
| 1 1 0 1 1 0 1 0 1 | | | | | | | | | | 1 0 0 1 1 | | | | | | | | | | | | | | |
| Product | | | | | | | | | | | | | | | | | | | | | | | | |

Figure 3: We add the multiplicand if the relevante Q-bit is '1'.

Shift-and-Add Multiply Example

| Multiplicand | | | | | | | | | | Multiplier | | | | | | | | | | | | | | | | | | | | | | | | |
|--------------|----|----|----|----|----|------|--|--|--|------------|----|----|----|----|-------------------------|------|------------|----|----|----|----|--------------------|----------------------------|------------------------------------|-------|--|---------------|--|--|---------------|--|-----------------|-----------------|---------------|
| C | B4 | B3 | B2 | B1 | B0 | | | | | | Q4 | Q3 | Q2 | Q1 | Q0 | | | | | | | | | | | | | | | | | | | |
| | 1 | 0 | 1 | 1 | 1 | (23) | | | | | 1 | 0 | 0 | 1 | 1 | (19) | | | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | Initial partial product | | | | | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | 1 | 0 | 0 | 1 | 1 | P0 | | | | | | | | | | Q0 = 1 -> Add | | | | |
| | | | | | | | | | | | | | | | | | | | | | | | | | Shift | | | | | | | | | |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | | | | | | 1 | 0 | 0 | 1 | 1 | P0+P1 x2^1 | | | | | | | | | | Q1 = 1 -> Add | | | | | | | |
| | | | | | | | | | | | | | | | | | | | | | | | | | Shift | | | | | | | | | |
| | | | | | | | | | | | | | | | 1 | 0 | 0 | 0 | 1 | 0 | 1 | P0+P1 x2^1+P2 x2^2 | | | | | | | | | | Q2 = 0 -> Shift | | |
| | | | | | | | | | | | | | | | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | P0+P1 x2^1+P2 x2^2+P3 x2^3 | | | | | | | | | | Q3 = 0 -> Shift | |
| | | | | | | | | | | | | | | | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | | | | | | | | | | | |
| | | | | | | | | | | | | | | | 1 | 0 | 1 | 1 | 1 | | | | | | | | | | | | | | | |
| | | | | | | | | | | | | | | | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | P0+P1 x2^1+P2 x2^2+P3 x2^3+P1 x2^4 | | | | | | | | | | Q1 = 1 -> Add |
| | | | | | | | | | | | | | | | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | Shift | | | | | | | | | |
| | | | | | | | | | | | | | | | A9 | A8 | A7 | A6 | A5 | A4 | A3 | A2 | A1 | A0 | | | | | | | | | | |
| | | | | | | | | | | | | | | | Product | | | | | | | | | | | | | | | | | | | |

Figure 4: Reorganise the rows. The 5 MSB are added only.

Hardware Multiplication

| | | |
|-----------|--------------|---|
| 23 | 10111 | Multiplicand |
| <u>19</u> | <u>10011</u> | Multiplier |
| | 00000 | Initial partial product |
| | <u>10111</u> | Add multiplicand, since multiplier bit is 1 |
| | 10111 | Partial product after add and before shift |
| | 010111 | Partial product after shift |
| | <u>10111</u> | Add multiplicand, since multiplier bit is 1 |
| | 1000101 | Partial product after add and before shift ^a |
| | 1000101 | Partial product after shift |
| | 01000101 | Partial product after shift |
| | 001000101 | Partial product after shift |
| | <u>10111</u> | Add multiplicand, since multiplier bit is 1 |
| | 110110101 | Partial product after add and before shift |
| 437 | 0110110101 | Product after final shift |

Figure 5: With overflow.

Shift-and-Add Multiply Example

| Clock | | Multiplicand | | | | | | Multiplier | | | | | | |
|-------|----|--------------|----|----|----|----|------|------------|----|----|----|----|------|------------------------------------|
| Cycle | | B4 | B3 | B2 | B1 | B0 | | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| | | 1 | 0 | 1 | 1 | 1 | (23) | 1 | 0 | 0 | 1 | 1 | (19) | |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| | | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | | Initial partial product |
| 1 | + | 1 | 0 | 1 | 1 | 1 | | | 1 | 0 | 0 | 1 | 1 | Q0 = 1 -> Add |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| | | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | | |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| 2 | sr | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | | P0 |
| 3 | + | 1 | 0 | 1 | 1 | 1 | | | 1 | 0 | 0 | 1 | 1 | Shift Q1 = 1 -> Add |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| | | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | | |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| 4 | sr | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | | P0+P1 x2^1 |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | Shift |
| 5 | sr | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | | P0+P1 x2^1+P2 x2^2 |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | Q2 = 0 -> Shift |
| 6 | sr | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | | P0+P1 x2^1+P2 x2^2+P3 x2^3 |
| 7 | + | 1 | 0 | 1 | 1 | 1 | | | 1 | 0 | 0 | 1 | 1 | Q3 = 0 -> Shift Q4 = 1 -> Add |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| | | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | | |
| | | C | A4 | A3 | A2 | A1 | A0 | Q4 | Q3 | Q2 | Q1 | Q0 | | |
| 8 | sr | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | | P0+P1 x2^1+P2 x2^2+P3 x2^3+P4 x2^4 |
| | | Product | | | | | | | | | | | | Shift |

Figure 6: Shows the Shift-Registers C-A-Q content

Binary Multiplier Schematic

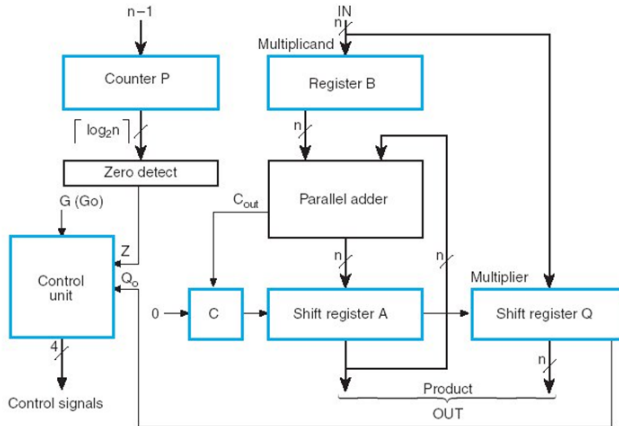


Figure 7: Including control.

Binary Multiplier Schematic

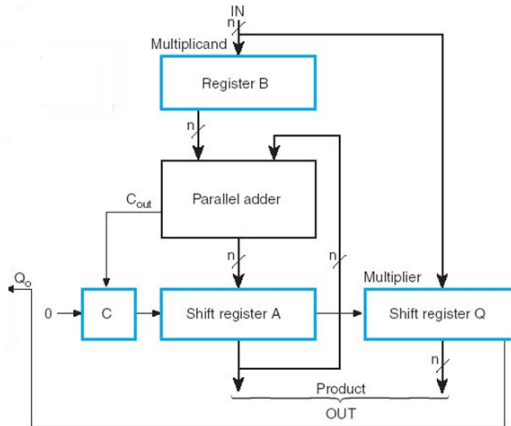


Figure 8: Without control.

Binary Multiplier Datapath Schematic

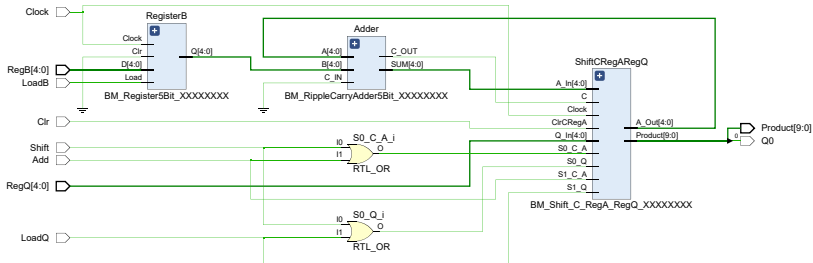


Figure 9: VHDL implementation.

Register B

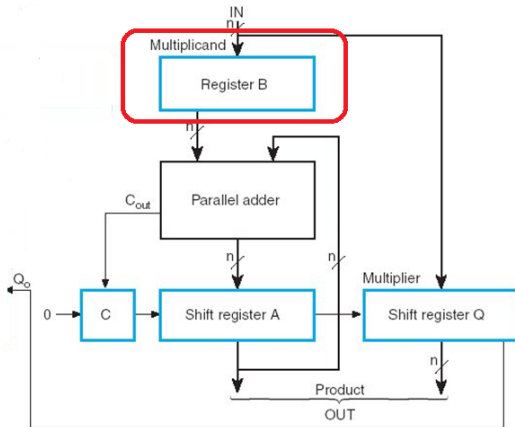


Figure 10: Register B holds the multiplicand.

Register B

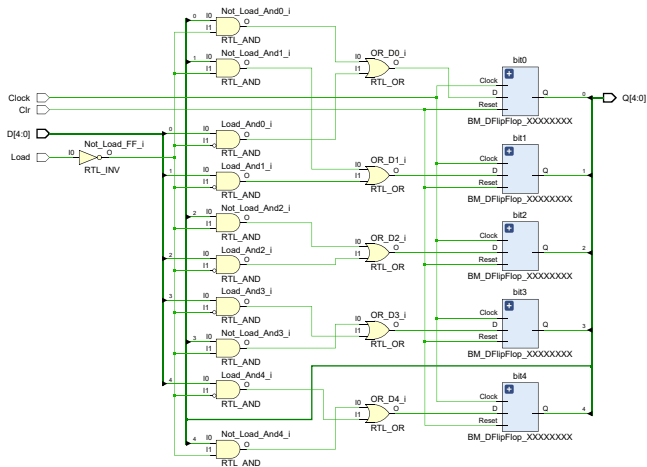


Figure 11: A 5-bit VHDL implementation.

Shift Registers A and B

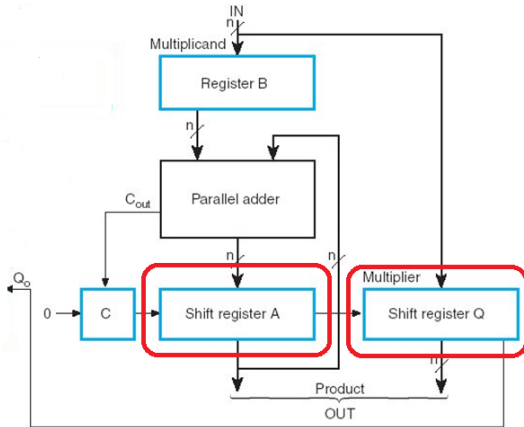


Figure 12: Shift Registers A needs to be cleared and Shift Registers Q holds the multiplier.

4-bit Shift Register Schematic



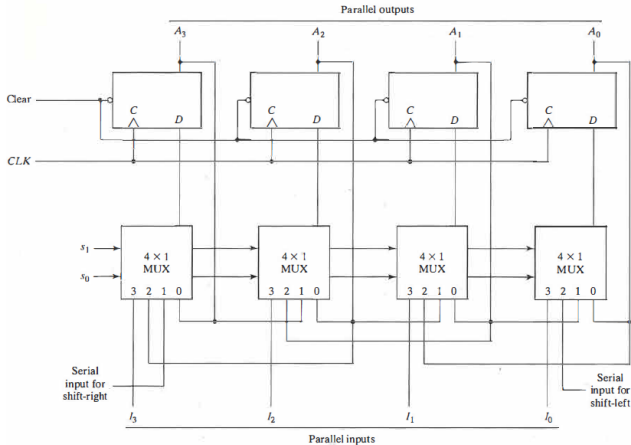


Figure 13: We can keep the content of the shift register, shift to the right, shift to the left, and parallel load the shift register.

5-bit VHDL Shift Register Implementation

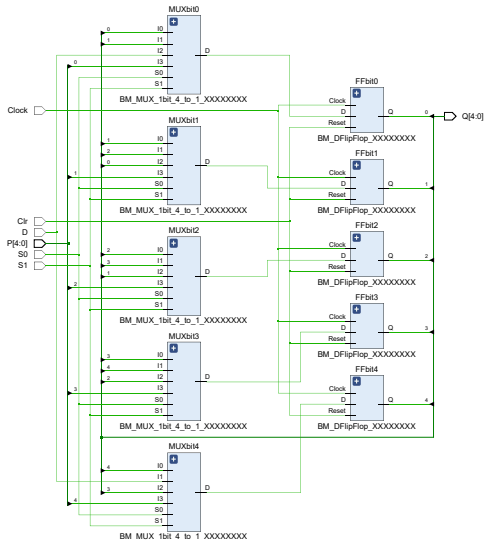

Shift Register's D-Flip-Flops

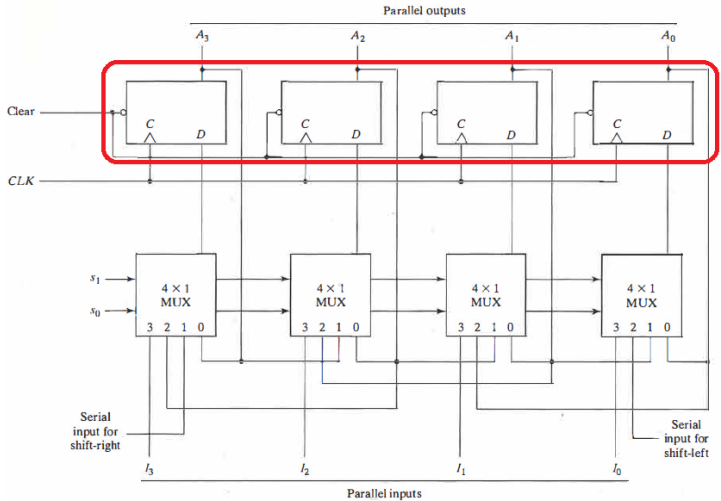

D-Flip-Flops without Reset

 


Figure 14: We implemented these so far.

D-Flip-Flops with Reset

 


Figure 15: The shift registers in this design require D-Flip-Flops with reset.

VHDL Implementation of a D-Flip-Flops with Reset



 


Figure 16: We require an AND-gate and a NAND-gate for every NAND-gate with three inputs. See figure 15.

Shift Register's 4 to 1 Multiplexer

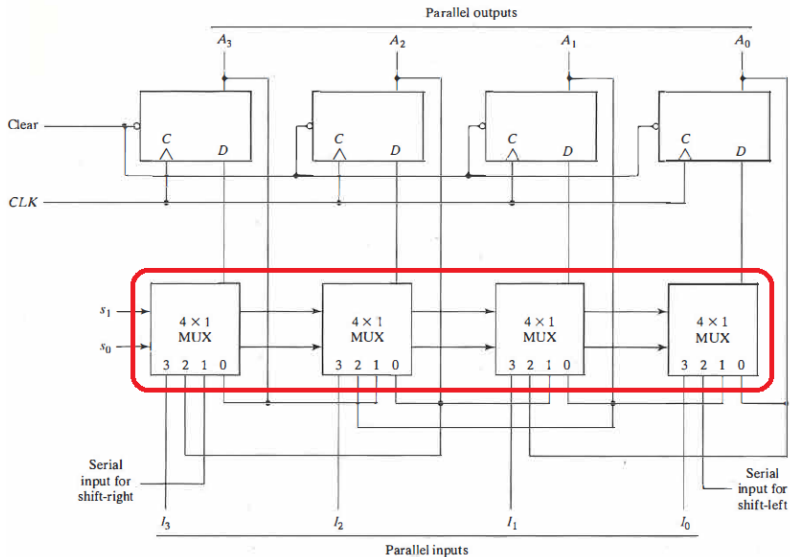

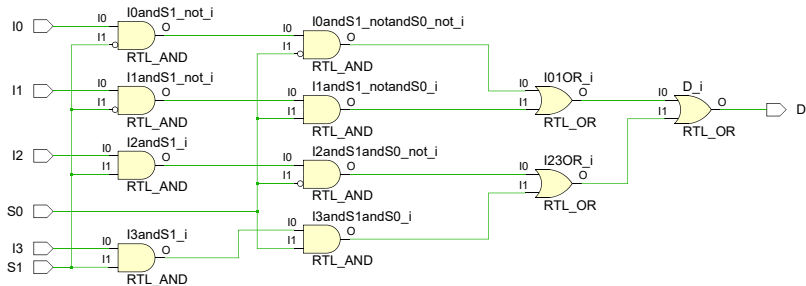VHDL Implementation of the 4 to 1 Multiplexer



Shift Flip-Flop


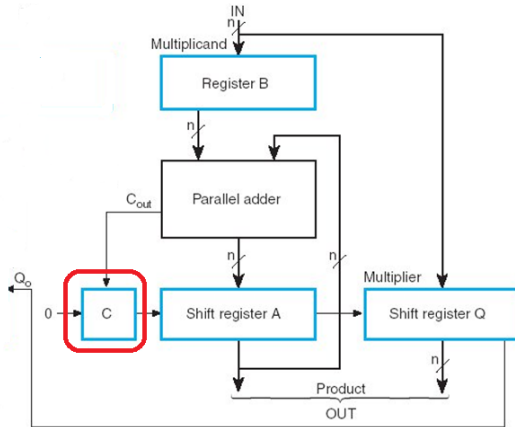


Figure 18: Similar to the Shift Register design with just one bit.

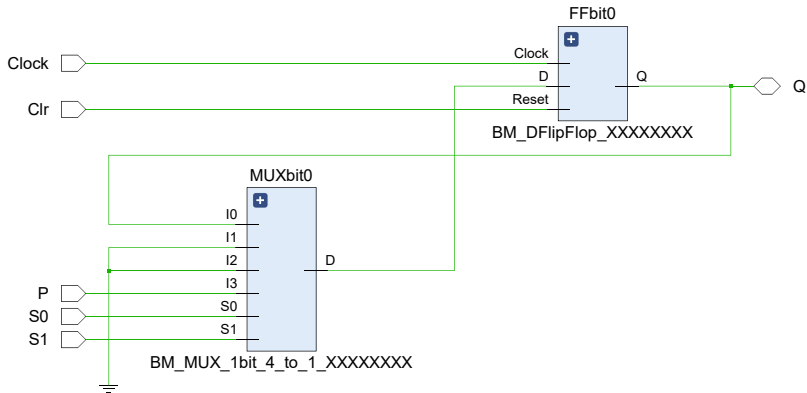VHDL Implementation of the Shift Flip-Flop



Shift Flip-Flop C and the Shift Registers A and Q



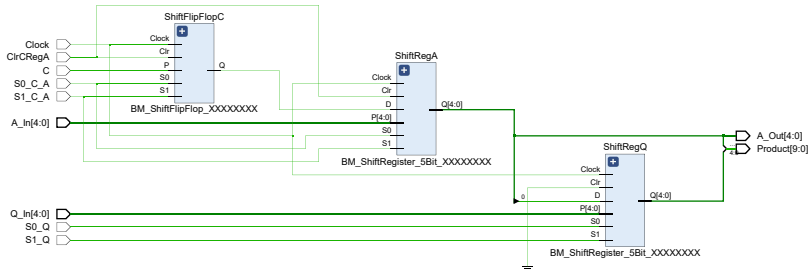


Figure 19: This design allows us to shift the Shift Flip-Flop C and the Shift Registers A and Q at the same time.

Parallel Adder

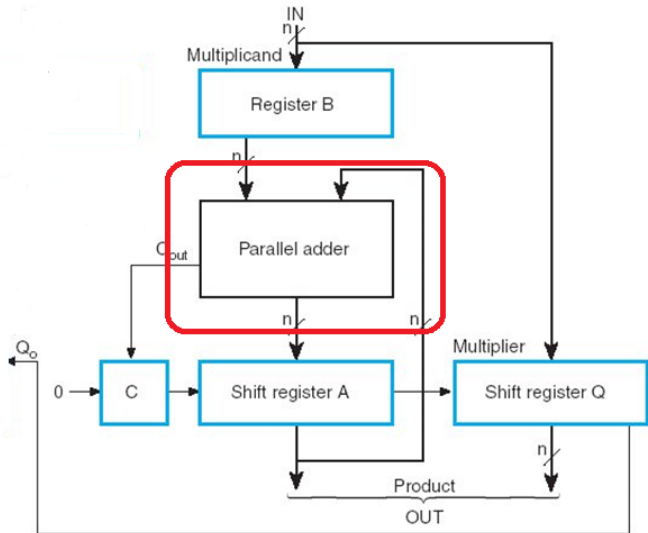

Full Adder

 

VHDL Implementation of the 5-bit Ripple Carry Adder

