


CSU11031

Problem Sheet 4

Q1

Calculate the voltage across each the resistor and the inductor in the following circuit where:

$$i(t) = 5 \sin(1000\pi t + \pi/3)$$

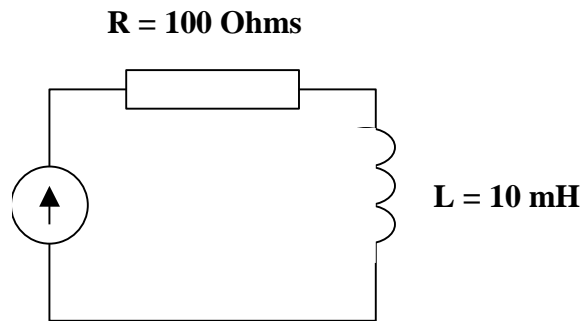

What is the total voltage across the load?

What is the total voltage at time $t = 0.02$ s?


What is the frequency of the applied current?

$500 \sin(1000\pi t + \pi/3) + 50\pi \cos(1000\pi t + \pi/3)V$, Substitute $t=0.02s$ into general expression, 500Hz

Q2

Calculate the current in each branch of the following circuit where:

$$v(t) = 20 \cos(1000\pi t + \pi/4)$$

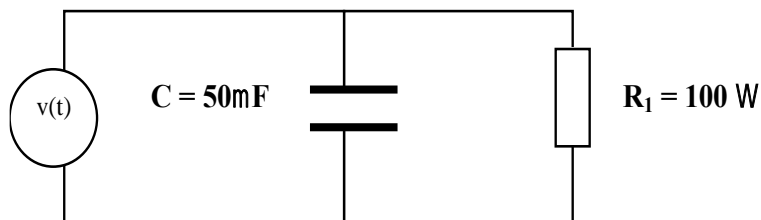


What is the total current in the circuit?

Capacitor: $-1000\pi \sin(1000\pi t + \pi/4)A$, Resistor: $0.2 \cos(1000\pi t + \pi/4)A$

Q3.

Calculate the voltage across R_C in the following circuit? Calculate the current in each branch.

$$v(t) = 10 \cos(500\pi t + \pi/6)$$

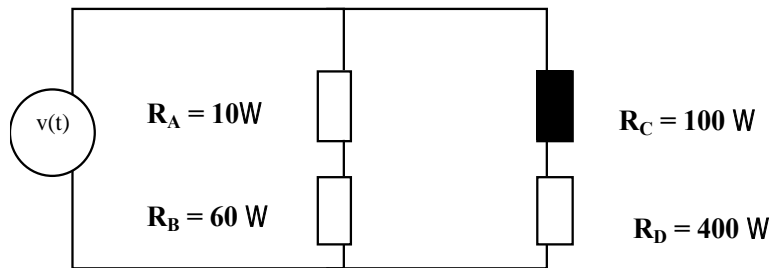

$$2\cos(500\pi t + \pi/6)V, 0.14\cos(500\pi t + \pi/6)A, 0.02\cos(500\pi t + \pi/6)A$$