

# CSU22022 Computer Architecture I

## Twelfth Lecture - Adder-Subtractor


---

Michael Manzke


2023-2024

Trinity College Dublin

# Adder-Subtractor (4-bit)

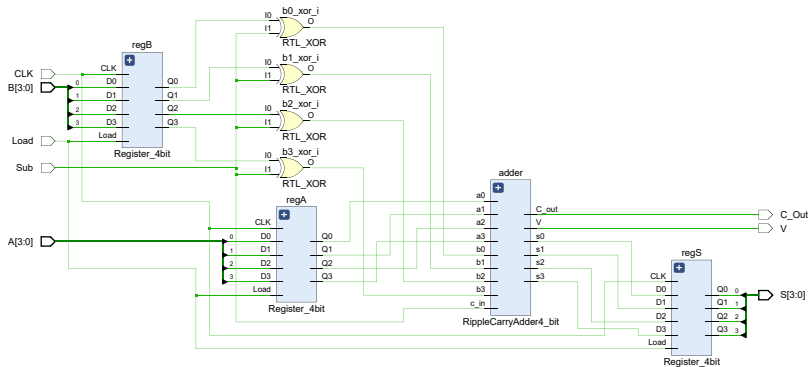

# How to subtract

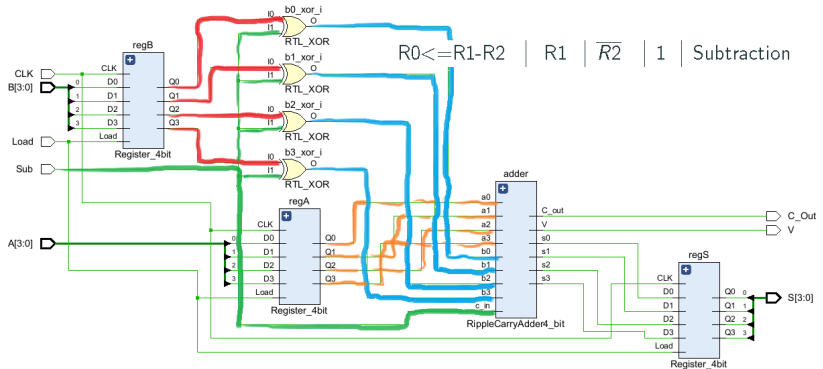


**Figure 1:** We use XOR-gates for every bit of the B-vector. If the signal "S"='0' a '1' remains a '1' and a '0' remains a '0', but if the signal "S"='1', a '1' becomes a '0' and a '0' becomes a '1'. Therefore, computing the 1's complement. Furthermore, we use the signal "S" to set the carry input signal "C" of the ripple carry adder. Therefore, adding a '1'. Consequently, we have the 1's Complement plus '1'. This makes 2's complement numbers negative if they were positive and positive numbers negative.

## 2's Complement Range of a n-bit Register $2^{n-1} - 1$ to $-2^{n-1}$

Two's Complement	Decimal		
$011_2$	$3_{10}$	$2^{n-1} - 1$	$2^{3-1} - 1 = 3$
$010_2$	$2_{10}$		
$001_2$	$1_{10}$		
$000_2$	$0_{10}$		
$111_2$	$-1_{10}$		
$110_2$	$-2_{10}$		
$101_2$	$-3_{10}$		
$100_2$	$-4_{10}$	$-2^{n-1}$	$-2^{3-1} = -4$


**Table 1:** For a fixed size register for arithmetic operands there is the hazard of overflow.

# Overflow and Carry $K_1 : C \leftarrow C_n, V \leftarrow C_n \oplus C_{n-1}$

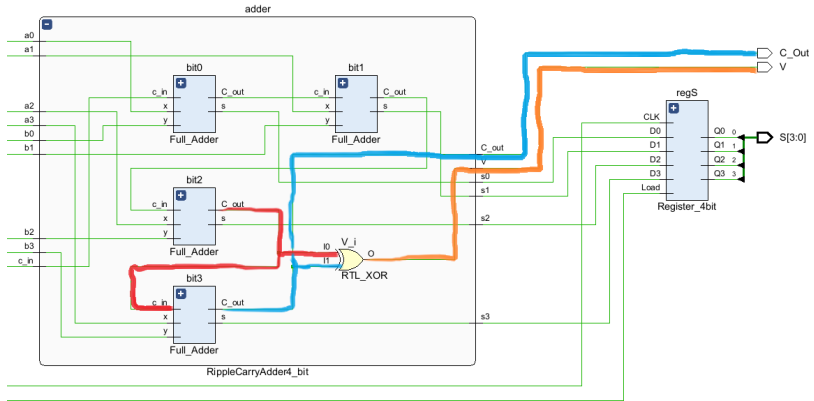

**Figure 2:** We can detect a overflow or a carry condition by recording the Status bits C=Carry and V=Overflow.

# Status Register - V, C, N, and Z Flags

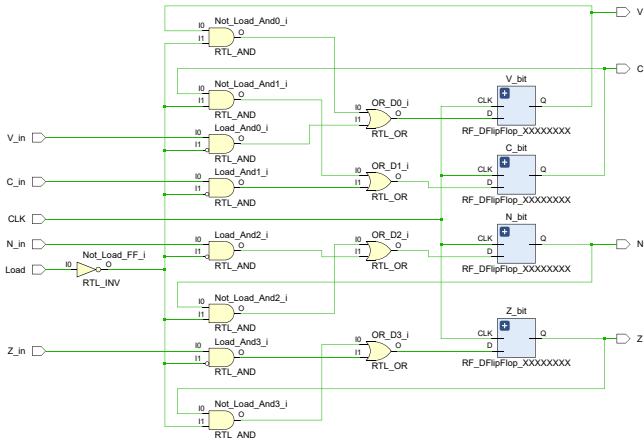

**Figure 3:** We should implement a status register to recording the Status bits C=Carry, V=Overflow, N=Negative, and Z=Zero. The Status flags allow to implement control flow.

# Status Register - One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Register_Status is
5     Port ( V_in, C_in, N_in, Z_in : in STD_LOGIC;
6           CLK, Load : in STD_LOGIC;
7           V, C, N, Z : out STD_LOGIC);
8 end Register_Status;
9
10 architecture Behavioral of Register_Status is
11
12     COMPONENT RF_DFlipFlop_XXXXXXX
13     Port ( CLK, D : in STD_LOGIC;
14           Q : out STD_LOGIC);
15     END COMPONENT;
```

Listing 1: entity Register\_Status

## Status Register - Two

```
1  signal Q_bit0, Q_bit1, Q_bit2, Q_bit3 : std_logic;
2  signal OR_D0, OR_D1, OR_D2, OR_D3 : std_logic;
3  signal Not_Load_FF, Load_FF : std_logic;
4  signal Not_Load_And0, Not_Load_And1, Not_Load_And2,
   Not_Load_And3 : std_logic;
5  signal Load_And0, Load_And1, Load_And2, Load_And3 :
   std_logic;
6
7  -- Propagation Delay according to StdentID e.g. 26 33
   57 25(DEC)
8  constant AND_gate_delay : Time := 6ns; -- 6 =5+1
9  constant NAND_gate_delay : Time := 3ns;-- 3=2+1
10 constant OR_gate_delay : Time := 8ns; -- 8=7+1
11 constant NOR_gate_delay : Time := 6ns; -- 6=5+1
12 constant XOR_gate_delay : Time := 4ns; -- 4=3+1
13 constant XNOR_gate_delay : Time := 4ns;-- 4=3+1
14 constant NOT_gate_delay : Time := 7ns; -- 7=6+1
```

Listing 2: signals and constants



## Status Register - Three

```
1 begin
2
3     Not_Load_FF <= not Load after NOT_gate_delay;
4     Load_FF <= not Not_Load_FF after NOT_gate_delay;
5
6     -- Instantiate the Overflow Status Bit V
7     V_bit: RF_DFlipFlop_XXXXXXX PORT MAP (
8         CLK => CLK, D => OR_D0, Q => Q_bit0 );
9
10    Not_Load_And0 <= Q_bit0 and Not_Load_FF after
11        AND_gate_delay;
12    OR_D0 <= Not_Load_And0 or Load_And0 after OR_gate_delay;
13    Load_And0 <= V_in and Load_FF after AND_gate_delay;
14    V <= Q_bit0;
```

Listing 3: Overflow Status Bit V

## Status Register - Four

```
1  -- Instantiate the Carry Status Bit C
2  C_bit: RF_DFlipFlop_XXXXXXX PORT MAP (
3      CLK => CLK, D => OR_D1, Q => Q_bit1 );
4
5  Not_Load_And1 <= Q_bit1 and Not_Load_FF after
6      AND_gate_delay;
7  OR_D1 <= Not_Load_And1 or Load_And1 after OR_gate_delay;
8  Load_And1 <= C_in and Load_FF after AND_gate_delay;
9  C <= Q_bit1;
10
11 -- Instantiate the Negative Status Bit N
12 N_bit: RF_DFlipFlop_XXXXXXX PORT MAP (
13     CLK => CLK, D => OR_D2, Q => Q_bit2);
14
15 Not_Load_And2 <= Q_bit2 and Not_Load_FF after
16     AND_gate_delay;
17 OR_D2 <= Not_Load_And2 or Load_And2 after OR_gate_delay;
18 Load_And2 <= N_in and Load_FF after AND_gate_delay;
19 N <= Q_bit2;
```


Listing 4: Status Bits C and N

## Status Register - Five

```
1  -- Instantiate the Zero Status Bit Z
2  Z_bit: RF_DFlopFlop_XXXXXXXX PORT MAP (
3      CLK => CLK, D => OR_D3, Q => Q_bit3);
4
5  Not_Load_And3 <= Q_bit3 and Not_Load_FF after
    AND_gate_delay;
6  OR_D3 <= Not_Load_And3 or Load_And3 after OR_gate_delay;
7  Load_And3 <= Z_in and Load_FF after AND_gate_delay;
8  Z <= Q_bit3;
9
10 end Behavioral;
```

Listing 5: Zero Status Bit Z

# Adder-Subtractor with Status Register

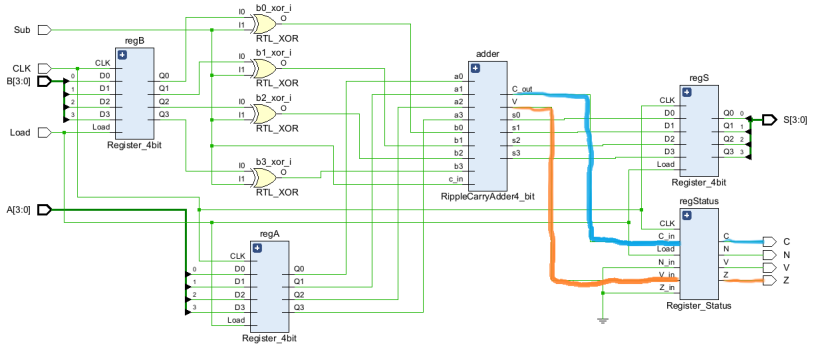

**Figure 4:** The status register is recording the Status bits C=Carry and V=Overflow. Also, we need to implement the N=Negative and Z=Zero.

This then is the basis for the adder-subtractor. The control input  $\overline{X}$  selects addition and  $X$  subtraction. In our example  $X$  is the "Sub" signal and  $K_1$  the Load signal.

$$\overline{X}.K_1 : R2 \leftarrow R0 + R1 \quad (1)$$

$$X.K_1 : R2 \leftarrow R0 + \overline{R1} + 1 \quad (2)$$


$$K_1 : C \leftarrow C_n, V \leftarrow C_n \oplus C_{n-1} \quad (3)$$

## 2's Complement N status Bit

Two's Complement	Decimal		
$011_2$	$3_{10}$	$2^{n-1} - 1$	$2^{3-1} - 1 = 3$
$010_2$	$2_{10}$		
$001_2$	$1_{10}$		
$000_2$	$0_{10}$		
$111_2$	$-1_{10}$		
$110_2$	$-2_{10}$		
$101_2$	$-3_{10}$		
$100_2$	$-4_{10}$	$-2^{n-1}$	$-2^{3-1} = -4$


**Table 2:** If the most significant bit (MSB) is a one we have a negative number.

# The N Status bit

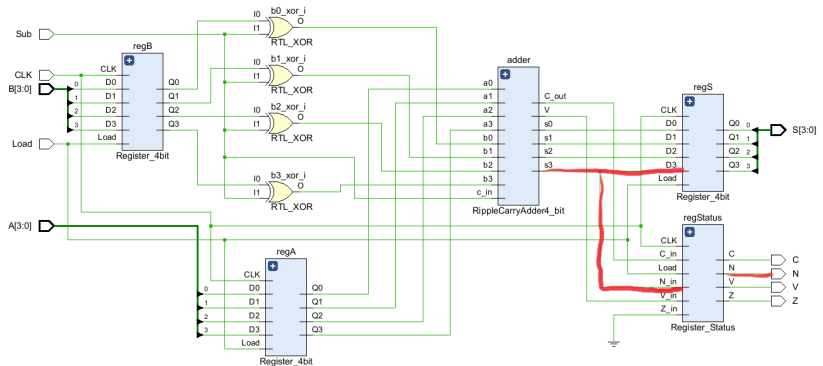

**Figure 5:** We connect the the MSB to the N-bit in the status register.


# The Z Status bit

 

**Figure 6:** We "or" together all sum-bits, "not" the output, and connect it to the Z-bit in the status register. Therefore, if all bits are zero the output is one.




## Add and Subtract Micro-operation

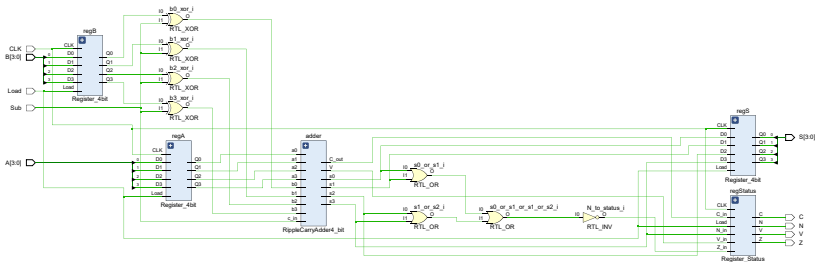

**Figure 7:** This synchronous circuit adds data from register B to data in register A or subtracts data from register B from data in register A and writes the result into register S. Furthermore, it calculates the status-flags V, C, N, and Z and writes these into the status register.

# Add-Subtract Micro-operation executed in 1 Clock Cycle

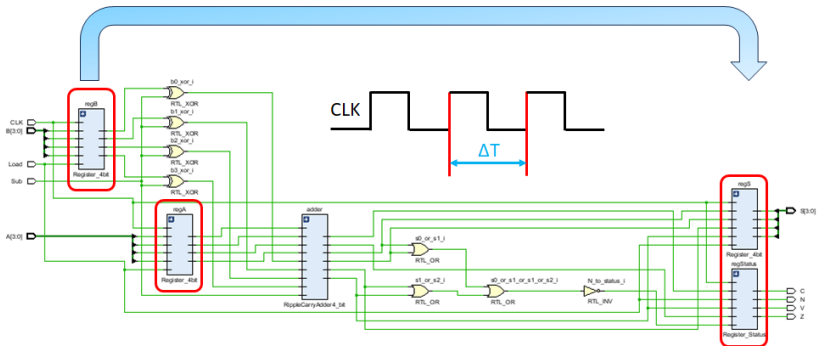

**Figure 8:** This circuit propagates data from registers A and B through the Ripple-Carry-Adder and its associated logic into register S and the status register in 1 clock cycle. The Ripple-Carry-Adder's and associated logic's worst case propagation delay plus the propagation delay of the receiving registers must be less than the  $\Delta T$  of the clock.