

CSU22022 Computer Architecture I

Sixth Lecture

Michael Manzke

2023-2024

Trinity College Dublin

Synchronous Sequential Logic

 


Figure 1: Block Diagram of Synchronous Sequential Logic

SR Latch

 


Figure 2: SR Latch Schematic

Latches are useful for asynchronous sequential circuits but not for synchronous sequential circuits.

SR Latch

	S	R	Q	Q'	Comment	Case
	0	0	0	0		A
Set	1	0	1	0		B
	0	0	1	0	after $S=1, R=0$	C
Reset	0	1	0	1		D
	0	0	0	1	after $S=0, R=1$	E
	1	1	0	0	undefined state	F
	0	0	x	x	undefined state	G

Table 1: SR Latch Function Table

SR Latch

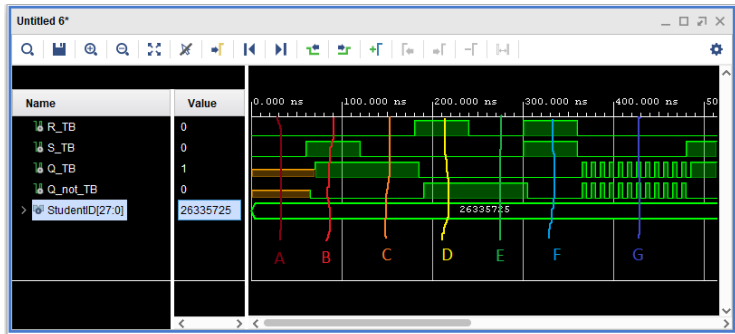


Figure 3: SR Latch Timing Diagram

Cases F and G lead to an undefined state.

SR Latch VHDL Code

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity SR_Latch is
5     Port ( R, S : in STD_LOGIC;
6           Q, Q_not : out STD_LOGIC);
7 end SR_Latch;
8
9 architecture Behavioral of SR_Latch is
10     signal Q_t, Q_not_t : std_logic;
11 begin
12     Q_t <= R nor Q_not_t after 5ns;
13     Q_not_t <= S nor Q_t after 5ns;
14     Q <= Q_t;
15     Q_not <= Q_not_t;
16 end Behavioral;
```

Listing 1: signals `Q_t` and `Q_not_t` are needed because you cannot use an out port as input.

SR Latch Test Bench VHDL Code - One

```
1 entity SR_Latch_TB is
2 -- we don't need ports
3 end SR_Latch_TB;
4 architecture Simulation of SR_Latch_TB is
5     -- Component Declaration for the Unit Under Test (UUT)
6     COMPONENT SR_Latch
7     Port ( R, S : in STD_LOGIC;
8           Q, Q_not : out STD_LOGIC);
9     END COMPONENT;
10    --Inputs Signals
11    signal R_TB, S_TB : STD_LOGIC := '0';
12    --Output Signal
13    signal Q_TB, Q_not_TB : STD_LOGIC := '0';
14    -- StudentID e.g. 26 33 57 25(DEC) = 1 91 D9 ED(HEX)
15    constant StudentID : STD_LOGIC_VECTOR (27 downto 0) := x"
        191D9ED";
```

Listing 2: SR Latch entity

SR Latch Test Bench VHDL Code - Two

```
1 begin
2
3   -- Instantiate the Unit Under Test (UUT)
4   uut: SR_Latch PORT MAP (
5       R => R_TB,
6       S => S_TB,
7       Q => Q_TB,
8       Q_not => Q_not_TB
9   );
```

Listing 3: Instantiate the Unit Under Test (UUT)

SR Latch Test Bench VHDL Code - Three

```
1  stim_proc: process
2      begin
3          S_TB <= '0'; R_TB <= '0';-- case A
4          wait for 60 ns;
5          S_TB <= '1'; R_TB <= '0';-- case B
6          wait for 60 ns;
7          S_TB <= '0'; R_TB <= '0';-- case C
8          wait for 60 ns;
9          S_TB <= '0'; R_TB <= '1';-- case D
10         wait for 60 ns;
11         S_TB <= '0'; R_TB <= '0';-- case E
12         wait for 60 ns;
13         S_TB <= '1'; R_TB <= '1';-- case F
14         wait for 60 ns;
15         S_TB <= '0'; R_TB <= '0';-- case G
16         wait for 60 ns;
17     end process;
18 end Simulation;
```

Listing 4: Input signals to the Unit Under Test (UUT)

D Latch

 


Figure 4: SR Latch Schematic

A **D Latch** can solve the problem with the undefined output.

D Latch

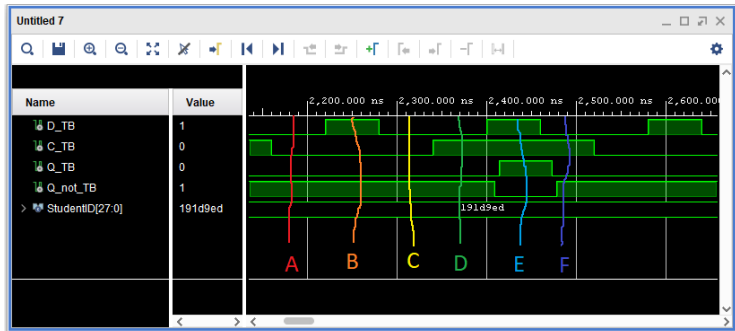


Figure 5: D Latch Timing Diagram

For case definitions see simulation code.

D Latch VHDL Code

```
1 entity D_Latch is
2     Port ( D, C : in STD_LOGIC;
3           Q, Q_not : out STD_LOGIC);
4 end D_Latch;
5
6 architecture Behavioral of D_Latch is
7     signal Q_t, Q_not_t, S, R, D_not : std_logic;
8 begin
9     S <= D and C after 4ns;
10    D_not <= not D after 3ns;
11    R <= C and D_not after 5ns;
12    Q_t <= R nor Q_not_t after 5ns;
13    Q_not_t <= S nor Q_t after 5ns;
14    Q <= Q_t;
15    Q_not <= Q_not_t;
16 end Behavioral;
```

Listing 5: signals `Q_t` and `Q_not_t` are needed because you cannot use an out port as input.

D Latch Test Bench VHDL Code - One

```
1 entity D_Latch_TB is
2   -- we don't need ports
3 end D_Latch_TB;
4
5 architecture Simulation of D_Latch_TB is
6   -- Component Declaration for the Unit Under Test (UUT)
7   COMPONENT D_Latch
8     Port ( D, C : in STD_LOGIC;
9           Q, Q_not : out STD_LOGIC);
10  END COMPONENT;
11  --Inputs Signals
12  signal D_TB, C_TB : STD_LOGIC := '0';
13  --Output Signal
14  signal Q_TB, Q_not_TB : STD_LOGIC := '0';
15  -- StudentID e.g. 26 33 57 25(DEC) = 1 91 D9 ED(HEX)
16  constant StudentID : STD_LOGIC_VECTOR (27 downto 0) := x"
    191D9ED";
```

Listing 6: SR Latch entity

D Latch Test Bench VHDL Code - Two

```
1 begin
2     -- Instantiate the Unit Under Test (UUT)
3     uut: D_Latch PORT MAP (
4         D => D_TB,
5         C => C_TB,
6         Q => Q_TB,
7         Q_not => Q_not_TB
8     );
```

Listing 7: Instantiate the Unit Under Test (UUT)

D Latch Test Bench VHDL Code - Three

```
1  stim_proc: process
2      begin
3          C_TB <= '0'; D_TB <= '0';-- case A
4          wait for 60 ns;
5          C_TB <= '0'; D_TB <= '1';-- case B
6          wait for 60 ns;
7          C_TB <= '0'; D_TB <= '0';-- case C
8          wait for 60 ns;
9          C_TB <= '1'; D_TB <= '0';-- case D
10         wait for 60 ns;
11         C_TB <= '1'; D_TB <= '1';-- case E
12         wait for 60 ns;
13         C_TB <= '1'; D_TB <= '0';-- case F
14         wait for 60 ns;
15
16     end process;
17 end Simulation;
```

Listing 8: Input signals to the Unit Under Test (UUT)

D-Type Positive-Edge-Triggered Flip-Flop

 


Figure 6: D-Type Positive-Edge-Triggered Flip-Flop Schematic

D-Type Positive-Edge-Triggered Flip-Flop

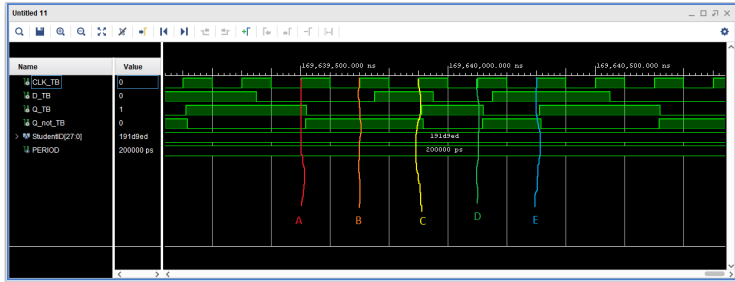


Figure 7: D-Type Positive-Edge-Triggered Flip-Flop Timing Diagram

For case definitions see simulation code.

D-Type Positive-Edge-Triggered Flip-Flop VHDL Code

```
1 entity D_Flip_Flop_PEdge is
2     Port ( CLK, D : in STD_LOGIC;
3           Q, Q_not : out STD_LOGIC);
4 end D_Flip_Flop_PEdge;
5 architecture Behavioral of D_Flip_Flop_PEdge is
6     signal Q_t, Q_not_t, X, S, R, Y, Z : std_logic;
7 begin
8     X <= Y nand S after 5ns;
9     S <= X nand CLK after 5ns;
10    Z <= S and CLK after 5ns;
11    R <= Z nand Y after 5ns;
12    Y <= R nand D after 5ns;
13    Q_t <= S nand Q_not_t after 5ns;
14    Q_not_t <= R nand Q_t after 5ns;
15    Q <= Q_t;
16    Q_not <= Q_not_t;
17 end Behavioral;
```

Listing 9: signals `Q_t` and `Q_not_t` are needed because you cannot use an out port as input.

D-Type Positive-Edge-Triggered Flip-Flop Test Bench VHDL Code - One

```
1  entity D_Flip_Flop_PEdge_TB is
2  -- we don't need ports
3  end D_Flip_Flop_PEdge_TB;
4  architecture Simulation of D_Flip_Flop_PEdge_TB is
5      -- Component Declaration for the Unit Under Test (UUT)
6      COMPONENT D_Flip_Flop_PEdge
7      Port ( CLK, D : in STD_LOGIC;
8            Q, Q_not : out STD_LOGIC);
9      END COMPONENT;
10     --Inputs Signals
11     signal CLK_TB, D_TB : STD_LOGIC := '0';
12     --Output Signal
13     signal Q_TB, Q_not_TB : STD_LOGIC := '0';
14     -- StudentID e.g. 26 33 57 25(DEC) = 1 91 D9 ED(HEX)
15     constant StudentID : STD_LOGIC_VECTOR (27 downto 0) := x"
16     191D9ED";
17     constant PERIOD : time := 200ns;
```

Listing 10: D-Type Positive-Edge-Triggered Flip-Flop entity

D-Type Positive-Edge-Triggered Flip-Flop Test Bench VHDL Code - Two

```
1 begin
2
3   -- Instantiate the Unit Under Test (UUT)
4   uut: D_Flip_Flop_PEdge PORT MAP (
5       CLK => CLK_TB,
6       D => D_TB,
7       Q => Q_TB,
8       Q_not => Q_not_TB
9   );
10
11   Clk_TB <= not CLK_TB after PERIOD/2;
```

Listing 11: Instantiate the Unit Under Test (UUT)

D-Type Positive-Edge-Triggered Flip-Flop Test Bench VHDL Code - Three

```
1  stim_proc: process
2  begin
3      wait until CLK_TB'event and CLK_TB='1';
4      D_TB <= '0' after PERIOD/4;           -- Case A
5      wait until CLK_TB'event and CLK_TB='1';
6      D_TB <= '0' after PERIOD/4;           -- Case B
7      wait until CLK_TB'event and CLK_TB='1';
8      D_TB <= '1' after PERIOD/4;           -- Case C
9      wait until CLK_TB'event and CLK_TB='1';
10     D_TB <= '0' after PERIOD/4;           -- Case D
11     wait until CLK_TB'event and CLK_TB='1';
12     D_TB <= '1' after PERIOD/4;           -- Case E
13     wait until CLK_TB'event and CLK_TB='1';
14 end process;
15 end Simulation;
```

Listing 12: Input signals to the Unit Under Test (UUT)