

CSU22022 Computer Architecture I

Fourth Lecture

Michael Manzke

2023-2024

Trinity College Dublin

3-to-8-Line-Decoder

x	y	z	D_i
0	0	0	D₀ = $x'y'z'$
0	0	1	D₁ = $x'y'z$
0	1	0	D₂ = $x'yz'$
0	1	1	D₃ = $x'yz$
1	0	0	D₄ = $xy'z'$
1	0	1	D₅ = $xy'z$
1	1	0	D₆ = xyz'
1	1	1	D₇ = xyz

Table 1: 3-to-8-Line-Decoder Truth Table

3-input Logic AND Gate

- The truth table 1 for the 3-to-8-Line-Decoder shows a need for a 3-input logic AND gate.

 


Figure 1: Two AND gates that implement a 3-input logic AND gate.

3-input Logic AND Gate VHDL Code

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity AND3inputs is
5     Port ( z : in STD_LOGIC;
6           y : in STD_LOGIC;
7           x : in STD_LOGIC;
8           D : out STD_LOGIC);
9 end AND3inputs;
10
11 architecture Behavioral of AND3inputs is
12     signal S0 : std_logic;
13 begin
14     S0 <= x and y after 8ns;
15     D <= S0 and z after 8ns;
16 end Behavioral;
```

Listing 1: This code implements the 3-input logic AND gate

3-to-8-Line-Decoder Schematic

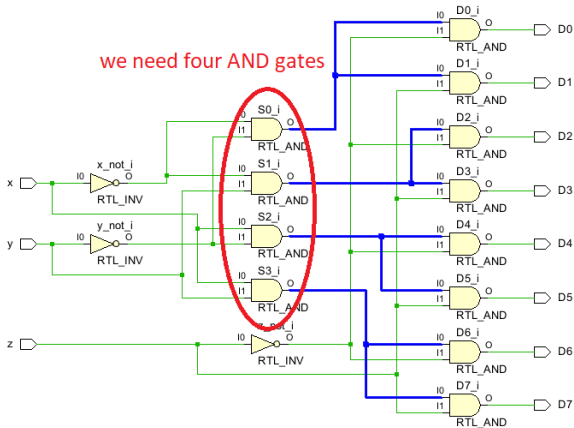


Figure 2: The truth table 1 shows that x and y are the same for D_0D_1 , D_2D_3 , D_4D_5 , and D_6D_7 . Therefore, we need four AND gates

3-to-8-Line-Decoder

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Decoder_3_to_8_Line is
5     Port ( x, y, z : in STD_LOGIC;
6           D0, D1, D2, D3, D4, D5, D6, D7 : out STD_LOGIC);
7 end Decoder_3_to_8_Line;
8
9 architecture Behavioral of Decoder_3_to_8_Line is
10
11     signal x_not, y_not, z_not : std_logic;
12     signal S0, S1, S2, S3 : std_logic;
```

Listing 2: entity

3-to-8-Line-Decoder

```
1 begin
2     x_not <= not x after 7ns;
3     y_not <= not y after 7ns;
4     z_not <= not z after 7ns;
5     S0 <= x_not and y_not after 8ns;
6     D0 <= S0 and z_not after 8ns;
7     D1 <= S0 and z after 8ns;
8     S1 <= x_not and y after 8ns;
9     D2 <= S1 and z_not after 8ns;
10    D3 <= S1 and z after 8ns;
11    S2 <= x and y_not after 8ns;
12    D4 <= S2 and z_not after 8ns;
13    D5 <= S2 and z after 8ns;
14    S3 <= x and y after 8ns;
15    D6 <= S3 and z_not after 8ns;
16    D7 <= S3 and z after 8ns;
17 end Behavioral;
```

Listing 3: Signal assignment statements

3-to-8-Line-Decoder Example

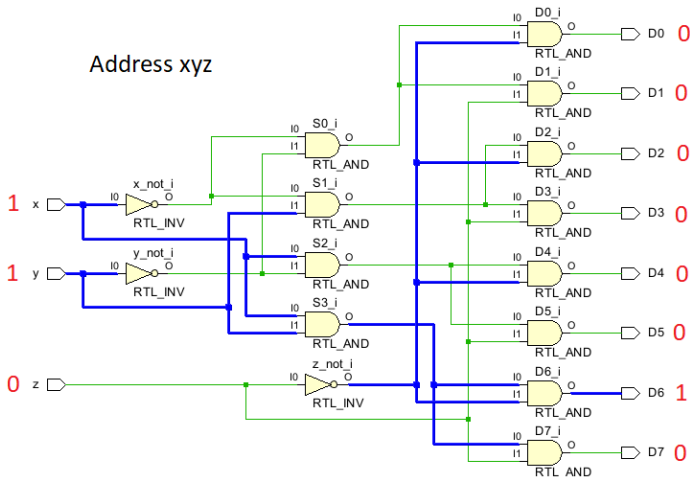


Figure 3: Address 110 selects D6

3-to-8-Line-Decoder another Example

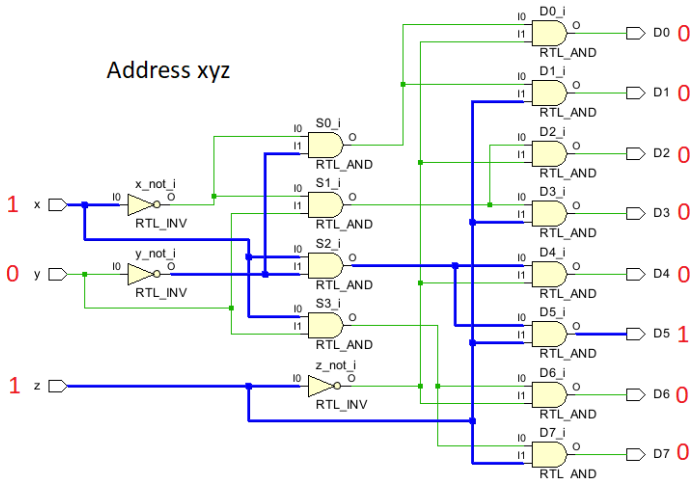


Figure 4: Address 101 selects D5

3-to-8-Line-Decoder Simulation Code One

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity Decoder_3_to_8_Line_TB is
5 -- we don't need ports
6 end Decoder_3_to_8_Line_TB;
7
8 architecture Simulation of Decoder_3_to_8_Line_TB is
9
10 -- Component Declaration for the Unit Under Test (UUT)
11
12     COMPONENT Decoder_3_to_8_Line
13     Port ( x, y, z : in STD_LOGIC;
14           D0, D1, D2, D3, D4, D5, D6, D7 : out STD_LOGIC);
15     END COMPONENT;
```

Listing 4: 3-to-8-Line-Decoder_TB entity

3-to-8-Line-Decoder Simulation Code Two

```
1  --Inputs  Signals
2  signal x_TB, y_TB, z_TB : STD_LOGIC := '0';
3
4  --Output  Signal
5  signal D0_TB, D1_TB, D2_TB, D3_TB : STD_LOGIC := '0';
6  signal D4_TB, D5_TB, D6_TB, D7_TB : STD_LOGIC := '0';
7
8  -- StudentID e.g. 26 33 57 25(DEC) = 1 91 D9 ED(HEX)
9  constant StudentID : STD_LOGIC_VECTOR (27 downto 0) := x"
    191D9ED";
```

Listing 5: signal and constant

3-to-8-Line-Decoder Simulation Code Three

```
1 begin
2
3   -- Instantiate the Unit Under Test (UUT)
4   uut: Decoder_3_to_8_Line PORT MAP (
5       x => x_TB,
6       y => y_TB,
7       z => z_TB,
8       D0 => D0_TB,
9       D1 => D1_TB,
10      D2 => D2_TB,
11      D3 => D3_TB,
12      D4 => D4_TB,
13      D5 => D5_TB,
14      D6 => D6_TB,
15      D7 => D7_TB
16   );
```

Listing 6: Port map for the Decoder_3_to_8_Line entity

3-to-8-Line-Decoder Simulation Code Four

```
1 stim_proc: process
2     begin
3         x_TB <= '0'; y_TB <= '0'; z_TB <= '0'; -- case A
4         wait for 60 ns;
5         x_TB <= '0'; y_TB <= '0'; z_TB <= '1'; -- case B
6         wait for 60 ns;
7         x_TB <= '0'; y_TB <= '1'; z_TB <= '0'; -- case C
8         wait for 60 ns;
9         x_TB <= '0'; y_TB <= '1'; z_TB <= '1'; -- case D
10        wait for 60 ns;
11        x_TB <= '1'; y_TB <= '0'; z_TB <= '0'; -- case E
12        wait for 60 ns;
13        x_TB <= '1'; y_TB <= '0'; z_TB <= '1'; -- case F
14        wait for 60 ns;
15        x_TB <= '1'; y_TB <= '1'; z_TB <= '0'; -- case G
16        wait for 60 ns;
17        x_TB <= '1'; y_TB <= '1'; z_TB <= '1'; -- case H
18        wait for 60 ns;
19    end process;
20 end Simulation;
```

3-to-8-Line-Decoder Timing Diagram


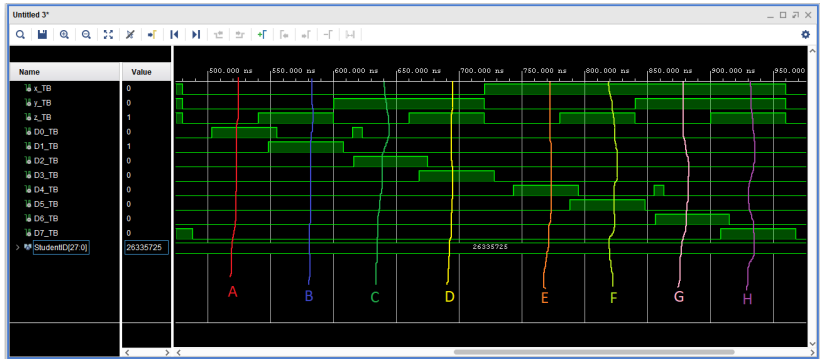


Figure 5: Cases A to H

Propagation Delay Example

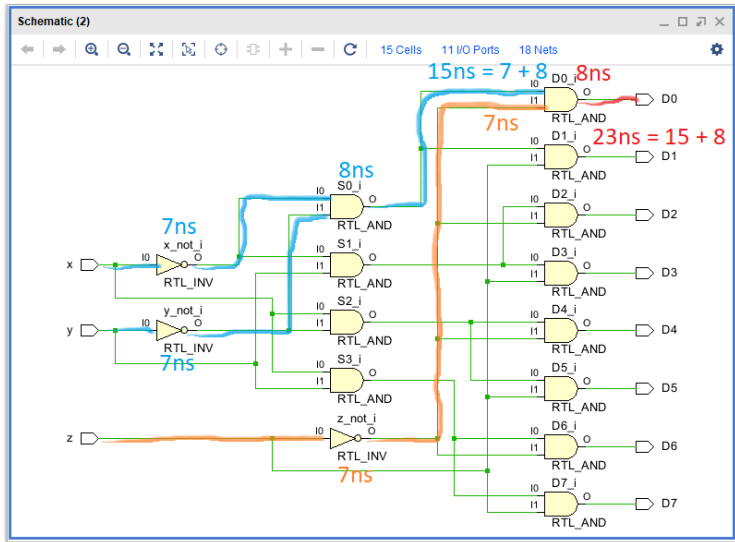

Decoder to select Register in the Register File

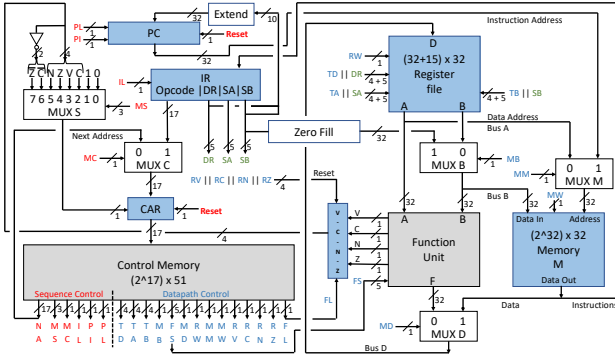


Figure 7: DR and TD provide the address for the decoder